

## 组成原理实验课程第 3 次实验报告

实验名称	定点乘法			班级	李涛老师
学生姓名	孙蒨	学号	2112060	指导老师	董前琨
实验地点	A308		实验时间	2023.4.4	

### 1、实验目的

- (1) 熟悉并掌握 MIPS 计算机中寄存器堆的原理和设计方法。
- (2) 初步了解 MIPS 指令结构和源操作数/目的操作数的概念。
- (3) 熟悉并运用 verilog 语言进行电路设计。
- (4) 为后续设计 cpu 的实验打下基础。

### 2、实验设备

- (1) 装有 Xilinx Vivado 的计算机一台。
- (2) LS-CPU-EXB-002 教学系统实验箱一套。


### 3、实验要求

- (1) 将原有的寄存器堆的写操作进行改进，使用 4 位 wen 控制信号，对应写入 wdata 的四个字节，比如 wen 为“1011”时，写入第 4、2、1 三个字节。
- (2) 将原有的寄存器堆的读操作进行改进，使用 2 位 ren 控制信号，控制读出数据的高 16 位和低 16 位。注意寄存器堆的两个读端口同时控制。
- (3) 本次实验不用仿真波形，直接上实验箱验证即可，注意八个拨码开关应都用上，wen 用 4 个，ren 用 2 个，input\_sel 用 2 个，上实验箱时请注意区分。


### 4. 实验内容说明

- (1) 学习 MIPS 计算机中寄存器堆的设计及原理，如：有多少个寄存器，有无特殊设置的寄存器，mips 指令如何去索引寄存器的等。
- (2) 自行设计本次实验的方案，画出结构框图，详细标出输入输出端口，本次实验建议设计为异步读同步写的寄存器堆，即读寄存器不需要时钟控制，但写寄存器需时钟控制。
- (3) 本次实验建议寄存器堆设计为 1 个写端口和 2 个读端口，后续 CPU 实验用到的寄存器堆需要 1 个写端口和 2 个读端口。
- (4) 根据设计的实验方案，使用 verilog 编写相应代码。
- (5) 对编写的代码进行仿真，得到正确的波形图。
- (6) 将以上设计作为一个单独的模块，设计一个外围模块去调用该模块，见图 4.1。外围模块中需调用封装好的 LCD 触摸屏模块，显示寄存器堆的读写端口地址和数据，最好能扫描出所有寄存器的值显示在 LCD 触摸屏上，并且需要利用触摸功能输入寄存器堆的读写地址和写数据。

### 5. 实验原理图

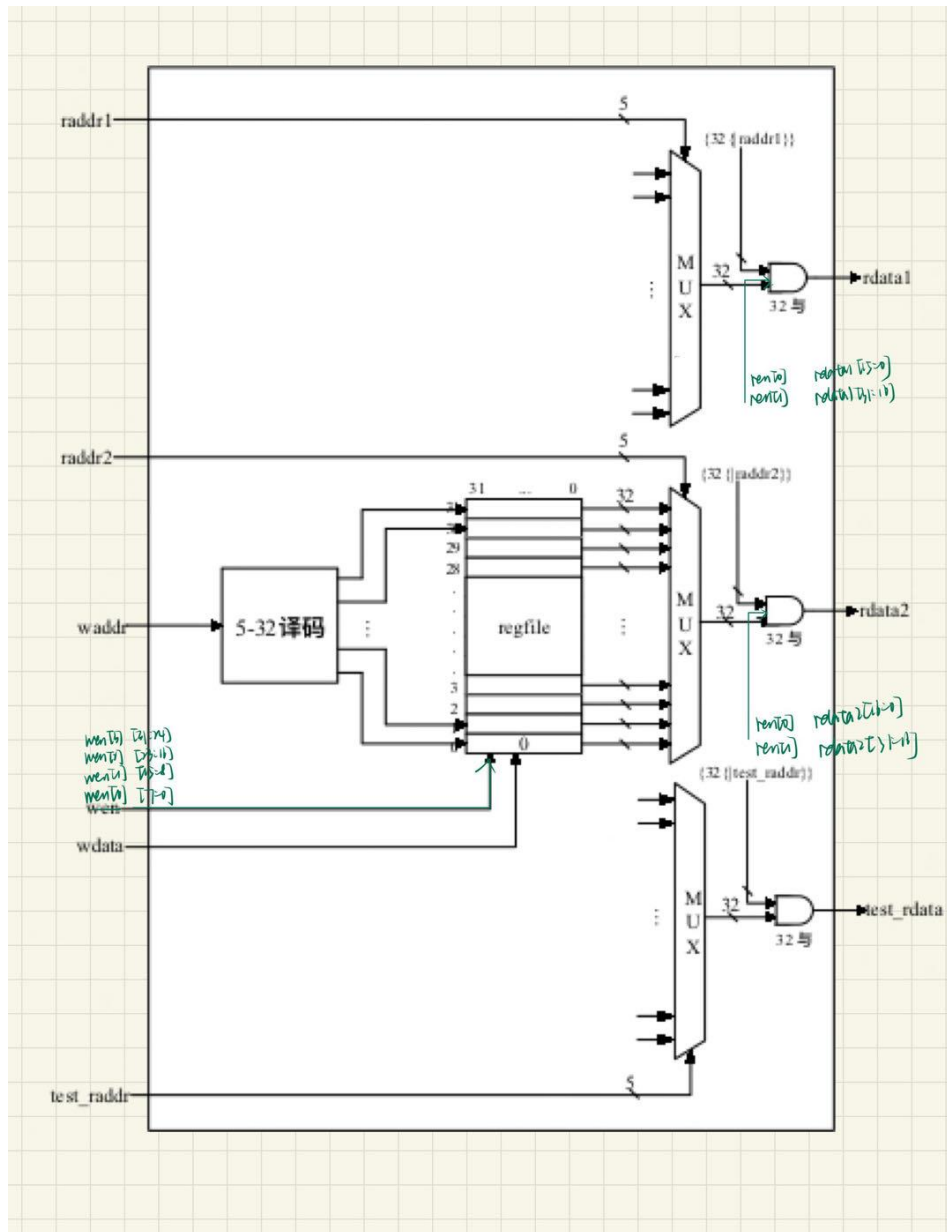

实验顶层模块框图：

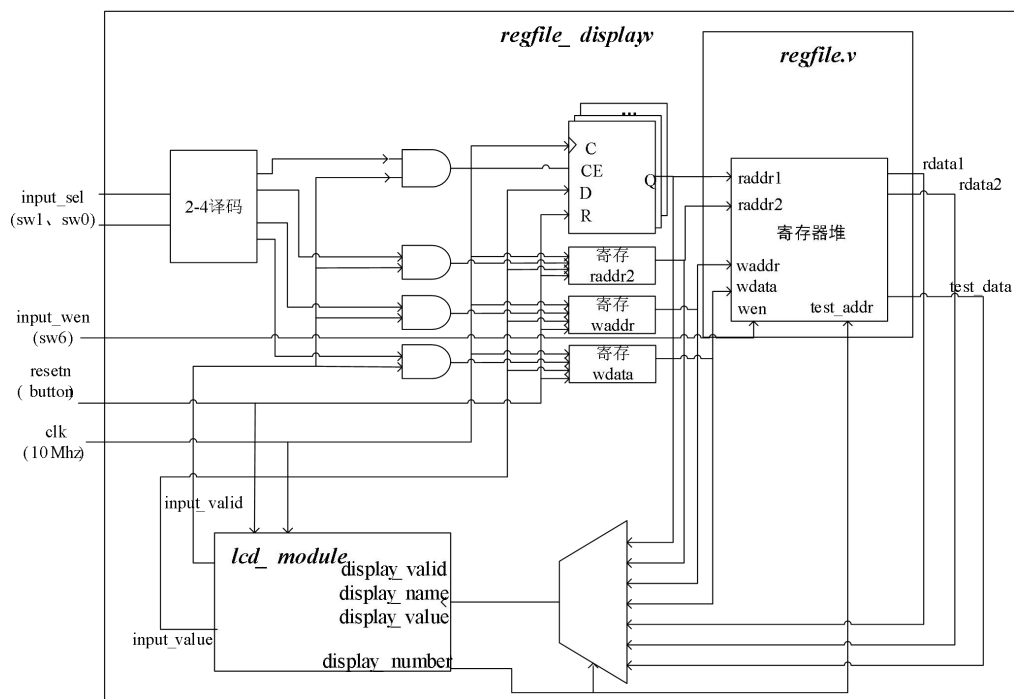

#### 4、实验步骤

##### A. regfile.v 修改

(1) regfile.v 修改，增加 2 位 ren 控制信号和 4 位 wen 控制信号

module regfile(
input clk,
input [3:0] wen,
input [1:0] ren,
input [4:0] raddr1,
input [4:0] raddr2,
input [4:0] waddr,
input [31:0] wdata,
output reg [31:0] rdata1,
output reg [31:0] rdata2,
input [4:0] test_addr,
output reg [31:0] test_data
);

(2) regfile.v 修改，wen 写操作

always @(posedge clk)
begin
if (wen[0])
rf[waddr][7:0] <= wdata[7:0];// 写使能控制字节 0 写入
else
rf[waddr][7:0] <= 8'd0;
if (wen[1])
rf[waddr][15:8] <= wdata[15:8];// 写使能控制字节 1 写入
else

	rf[waddr][15:8] <= 8'd0;
	if (wen[2])
	rf[waddr][23:16] <= wdata[23:16];// 写使能控制字节 2 写入
	else
	rf[waddr][23:16] <= 8'd0;
	if (wen[3])
	rf[waddr][31:24] <= wdata[31:24];// 写使能控制字节 3 写入
	else
	rf[waddr][31:24] <= 8'd0;
	end

判断 wen[i] 的值，如果为 1 的话，将第 i 字节的值写入寄存器。如果 wen[0] 是 1，写入寄存器的最低字节；如果 wen[1] 是 1，写入寄存器的次低字节；如果 wen[2] 是 1，写入寄存器的次高字节；如果 wen[3] 是 1，写入寄存器的最高字节。

### (3) regfile.v 修改，ren 读操作

	always @(*)
	begin
	if (ren[0])
	rdata1[15:0] <= rf[raddr1][15:0];//控制低 16 位读取
	else
	rdata1[15:0] <= 16'd0;
	if (ren[1])
	rdata1[31:16] <= rf[raddr1][31:16];//控制高 16 位读取
	else
	rdata1[31:16] <= 16'd0;
	end
	//读端口 2
	always @(*)
	begin
	if (ren[0])
	rdata2[15:0] <= rf[raddr2][15:0];//控制低 16 位读取
	else
	rdata2[15:0] <= 16'd0;
	if (ren[1])
	rdata2[31:16] <= rf[raddr2][31:16];//控制高 16 位读取
	else
	rdata2[31:16] <= 16'd0;
	end

判断 ren[i] 的值，如果 ren[0] 为 1，读寄存器后 16 位内容；如果 ren[1] 为 1，读寄存器前 16 位内容。

### B. regfile\_display.v 修改

#### (1) 修改 regfile\_display.v 文件，增加 wen[3:0]，ren[1:0] 的拨码开关和 led 显示

	module regfile_display(
	//时钟与复位信号

	input clk,
	input resetn, //后缀"n"代表低电平有效
	//拨码开关，用于产生写使能、读使能 and 选择输入数
	input [3:0] wen,
	input [1:0] ren,
	input [1:0] input_sel,
	//led 灯，用于指示写使能、读使能信号，和正在输入什么数据
	output led_wen0,
	output led_wen1,
	output led_wen2,
	output led_wen3,
	output led_ren0,
	output led_ren1,
	output led_waddr, //指示输入写地址
	output led_wdata, //指示输入写数据
	output led_raddr1, //指示输入读地址 1
	output led_raddr2, //指示输入读地址 2

(2) 修改 regfile\_display.v 文件，增加 wen 和 ren 的 led 显示

	assign led_wen0 = (wen[0]==1);
	assign led_wen1 = (wen[1]==1);
	assign led_wen2 = (wen[2]==1);
	assign led_wen3 = (wen[3]==1);
	assign led_ren0 = (ren[0]==1);
	assign led_ren1 = (ren[1]==1);
	assign led_raddr1 = (input_sel==2'd0);
	assign led_raddr2 = (input_sel==2'd1);
	assign led_waddr = (input_sel==2'd2);
	assign led_wdata = (input_sel==2'd3);
	//----{LED 显示}end

(3) 修改 regfile\_display.v 文件，修改 regfile 模块

	regfile rf_module(
	.clk (clk ),
	.wen (wen ),
	.ren (ren),
	.raddr1(raddr1),
	.raddr2(raddr2),
	.waddr (waddr ),
	.wdata (wdata ),
	.rdata1(rdata1),
	.rdata2(rdata2),
	.test_addr(test_addr),

	.test_data(test_data)
	);
	//----{调用寄存器堆模块}end

### C. 修改 regfile.xdc 文件

(1) led 灯连接，用于输出

	#led 灯连接，用于输出
	set_property PACKAGE_PIN H7 [get_ports led_wen3]
	set_property PACKAGE_PIN D5 [get_ports led_wen2]
	set_property PACKAGE_PIN A3 [get_ports led_wen1]
	set_property PACKAGE_PIN A5 [get_ports led_wen0]
	set_property PACKAGE_PIN A4 [get_ports led_ren1]
	set_property PACKAGE_PIN F7 [get_ports led_ren0]
	set_property PACKAGE_PIN D5 [get_ports led_waddr]
	set_property PACKAGE_PIN A3 [get_ports led_wdata]
	set_property PACKAGE_PIN A5 [get_ports led_raddr1]
	set_property PACKAGE_PIN A4 [get_ports led_raddr2]

(2) 拨码开关连接，用于输入

	#拨码开关连接，用于输入，依次为 sw0,sw1,sw7
	set_property PACKAGE_PIN AC21 [get_ports wen[3]]
	set_property PACKAGE_PIN AD24 [get_ports wen[2]]
	set_property PACKAGE_PIN AC22 [get_ports wen[1]]
	set_property PACKAGE_PIN AC23 [get_ports wen[0]]
	set_property PACKAGE_PIN AB6 [get_ports ren[1]]
	set_property PACKAGE_PIN W6 [get_ports ren[0]]
	set_property PACKAGE_PIN AA7 [get_ports input_sel[1]]
	set_property PACKAGE_PIN Y6 [get_ports input_sel[0]]
	set_property IOSTANDARD LVCMOS33 [get_ports clk]
	set_property IOSTANDARD LVCMOS33 [get_ports resetn]
	set_property IOSTANDARD LVCMOS33 [get_ports led_wen3]
	set_property IOSTANDARD LVCMOS33 [get_ports led_wen2]
	set_property IOSTANDARD LVCMOS33 [get_ports led_wen1]
	set_property IOSTANDARD LVCMOS33 [get_ports led_wen0]
	set_property IOSTANDARD LVCMOS33 [get_ports led_ren1]
	set_property IOSTANDARD LVCMOS33 [get_ports led_ren0]
	set_property IOSTANDARD LVCMOS33 [get_ports led_raddr1]
	set_property IOSTANDARD LVCMOS33 [get_ports led_raddr2]
	set_property IOSTANDARD LVCMOS33 [get_ports led_waddr]
	set_property IOSTANDARD LVCMOS33 [get_ports led_wdata]
	set_property IOSTANDARD LVCMOS33 [get_ports wen]
	set_property IOSTANDARD LVCMOS33 [get_ports input_sel[1]]
	set_property IOSTANDARD LVCMOS33 [get_ports input_sel[0]]

led 灯从左到右依次为 wen[3], wen[2], wen[1], wen[0], ren[1], ren[0], 是否输入写地址，

是否输入写数据，是否输入读地址 1，是否输入读地址 2。


拨码开关从左到右依次为 wen[3], wen[2], wen[1], wen[0], ren[1], ren[0], input\_sel[1], input\_sel[0]。

## 5、实验结果分析

### (1) 输入 12345678



### (2) 拨码开关 1

 


### (3) 拨码开关 2






(4) 拨码开关 3

 


(5) 拨码开关 4




 


(6) 拨码开关 5

 

(7) 拨码开关 6

 


(7) 拨码开关 1、3

 


(8) 拨码开关 1、7




 

(8) 拨码开关 1、8

 

(9) 再拨动拨码开关 3

 

## 6、总结感想

在原有的寄存器堆实现的基础上，实现了对写操作和读操作的改进。通过 wen 控制信号的四位，实现对 wdata 的四个字节的选择性写入；通过 ren 控制信号的两位，实现对 rdata1 和 rdata2 的高 16 位和低 16 位的选择性输出。同时，注意到寄存器堆的两个读端口需要同时控制。